

Tutorial

1. Calculate intrinsic carrier concentration (conc.) of germanium at 30°C.

$$\underline{\text{Sol}^u}$$

$$n_i = B \cdot T^{\frac{3}{2}} \cdot e^{\left(\frac{-E_g}{2kT}\right)}$$

$$= (1.66 \times 10^{15}) \times (30 + 273)^{1.5} \times e^{\frac{-0.66}{2 \times 86.17 \times 10^{-6} \times 300}}$$

$$= (2.83 \times 10^{13}) \text{ per cm}^3$$

(Ans)

2. A Si block is at 300K, which is doped with Boron of conc. $5.6 \times 10^{18} \text{ cm}^{-3}$. Calculate the concentration of e^- & h^+ at thermal equilibrium.

$$\underline{\text{Sol}^m}$$

$$T = 300 \text{ K} ; N_a = 5.6 \times 10^{18} \text{ cm}^{-3}$$

$$n_i = B \cdot T^{\frac{3}{2}} \cdot e^{\frac{-E_g}{2kT}}$$

$$= 5.23 \times 10^{15} \times 300^{1.5} \times e^{\frac{-1.1}{2 \times 86.17 \times 10^{-6} \times 300}}$$

$$= 1.5 \times 10^{10} \text{ cm}^{-3}$$

Now, B doping means tri-valent impurity addition, which further means p-type extrinsic material.

$$\therefore N_a \gg n_i$$

$$\therefore p_0 \approx N_a = 5.6 \times 10^{18} \text{ cm}^{-3}$$

(Ans)

We know,

$$n_o = \frac{n_i^2}{p_0} = \frac{n_i^2}{N_a} = \frac{(1.5 \times 10^{10})^2}{5.6 \times 10^{18}}$$

$$= 40.17 \text{ cm}^{-3}$$

(Ans)

3. Consider a Si block at 300°K that has been doped with 'P' atoms. Assume, $\mu_n = 1380 \text{ cm}^2/\text{V-s}$, $\mu_p = 480 \text{ cm}^2/\text{V-s}$, $E = 220 \text{ V/cm}$, & $N_d = 9.1 \times 10^{16} \text{ cm}^{-3}$. Calculate drift current density.

Soln. 'P' doping means pentavalent, which leads to n-type.
 $\therefore n \approx N_d = 9.1 \times 10^{16} \text{ cm}^{-3}$ (Majority conc.)
 $\& p = \frac{n^2}{N_d} = \frac{(1.5 \times 10^{10})^2}{9.1 \times 10^{16}} = 2.47 \times 10^3 \text{ cm}^{-3}$ (Minority conc.)

As, $N_d \gg p$, or $n \gg p$

$$\begin{aligned}\text{Conductivity, } \sigma &= q \cdot \mu_n \cdot n + q \cdot \mu_p \cdot p \approx q \cdot \mu_n \cdot n \\ &= (1.6 \times 10^{-19})(1380)(9.1 \times 10^{16}) \\ &= 20.09 \text{ per Ohm-cm} \\ &= 20.09 / \Omega \text{-cm}\end{aligned}$$

We know,

$$\begin{aligned}\text{drift current density: } J &= \sigma \cdot E \\ &= (20.09)(220) \\ &= 4.42 \times 10^3 \text{ A/cm}^2 \\ &\quad (\text{Ans})\end{aligned}$$

4. A block of Si has e^- concentration that linearly varies from $n = 10^{13} \text{ cm}^{-3}$ to 10^{18} cm^{-3} over a distance $x = 0.1 \text{ to } 4 \mu\text{m}$. If $T = 27^\circ\text{C}$ & diffusion co-efficient $D_n = 36 \text{ cm}^2/\text{s}$, calculate diffusion I-density:

$$\begin{aligned}\text{Soln. We know, } J_n &= q \cdot D_n \cdot \frac{dn}{dx} = q \cdot D_n \cdot \frac{\Delta n}{\Delta x} \\ &= (1.6 \times 10^{-19})(36) \left(\frac{10^{18} - 10^{13}}{4 \times 10^{-4} - 0.1 \times 10^{-4}} \right) \\ &= 14.76 \times 10^3 \text{ A/cm}^2 \quad (\text{Ans})\end{aligned}$$

5. Calculate V_{bi} & C_j of a Ge p-n junction diode at $30^\circ C$. Assume, $N_a = 10^{17} \text{ cm}^{-3}$, $N_d = 10^{15} \text{ cm}^{-3}$, $C_{jo} = 0.5 \text{ pF}$, reverse biased voltage $V_R = 1.1 \text{ V}$ & 4.5 V .



Solⁿ We know, $n_i = B \cdot T^{3/2} \cdot e^{\frac{-E_g}{2kT}}$

@ $30^\circ C$ for Ge, $n_i = 2.83 \times 10^{13} \text{ cm}^{-3}$

We know, $V_T \approx 26 \text{ mV} @ 300K$

$$V_{bi} = \left(\frac{kT}{q} \right) \ln \left[\frac{N_a N_d}{n_i^2} \right]$$

$$= \left[\frac{1.38 \times 10^{-23} \times 303}{1.6 \times 10^{-19}} \right] \ln \left[\frac{10^{17} \cdot 10^{15}}{(2.83 \times 10^{13})^2} \right]$$

$$= 0.306 \text{ V} \quad (\text{Ans})$$

We know,

$$C_j = C_{jo} \left(1 + \frac{V_R}{V_{bi}} \right)^{-\frac{1}{2}}$$

$$= (0.5 \times 10^{-12}) \left(1 + \frac{1.1}{0.306} \right)^{-\frac{1}{2}}$$

$$= 233.25 \text{ fF} \quad [\text{@ } V_R = 1.1 \text{ V}] \quad (\text{Ans})$$

$$\text{Also, } C_j = (0.5 \times 10^{-12}) \left(1 + \frac{4.5}{0.306} \right)^{-\frac{1}{2}}$$


$$= 126.16 \text{ fF} \quad [\text{@ } V_R = 4.5 \text{ V}]$$

6. Consider all the given & calculated parameters in the previous problem. Calculate time constants if a high pass filter like ckt is realized by using a $10 \text{ M}\Omega$ resistor and the diode.

$$\text{Soln. } \tau = R.C$$

$$T_1 = 10 \times 10^6 \times 233.25 \times 10^{-15}$$

$$= 2.33 \mu\text{s}$$

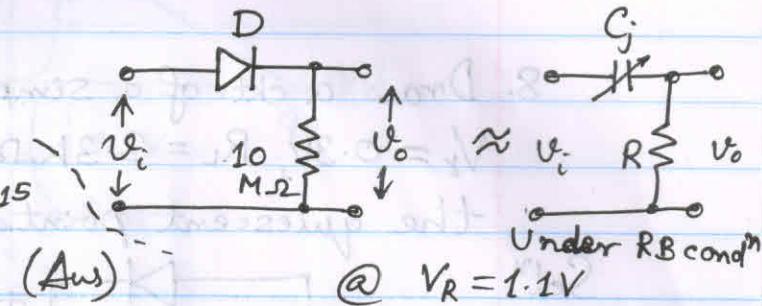

(Ans)

@ $V_R = 1.1V$

$$T_2 = 10 \times 10^6 \times 126.16 \times 10^{-15}$$

$$= 1.26 \mu\text{s}$$

(Ans)

@ $V_R = 4.5V$

7. Calculate diode voltages while current flowing through it is $+4.2 \text{ mA}$ & $+1.2 \times 10^{-14} \text{ A}$. Assume, $T = 300K$, $I_S = 10^{-14} \text{ A}$, $n = 1$. Find the material of the diode.

$$\text{Soln. We know, } i_D = I_S \left[e^{\frac{V_D}{nV_T}} - 1 \right]$$

$$\Rightarrow e^{\frac{V_D}{V_T}} = \frac{i_D}{I_S} + 1$$

$$\Rightarrow \frac{V_D}{V_T} = \ln \left[\frac{i_D}{I_S} + 1 \right]$$

$$\Rightarrow V_D = V_T \ln \left[\frac{i_D}{I_S} + 1 \right]$$

$$\text{At, } i_D = 4.2 \text{ mA},$$

$$V_D = (26 \text{ mV}) \ln \left(\frac{4.2 \text{ mA}}{10^{-14}} + 1 \right) = 0.6958 \text{ V}$$


$$\text{At, } i_D = +1.2 \times 10^{-14} \text{ A},$$

$$V_D = (26 \times 10^{-3}) \ln \left[\frac{+1.2 \times 10^{-14}}{10^{-14}} + 1 \right] = +0.0204 \text{ V}$$

Since, $V_D \approx 0.7V$, the diode is made of Si.

8. Draw a ckt. of a simple half wave rectifier. Let, $V_f = 0.3V$, $R_L = 3.3k\Omega$, $V_i(\text{AC}) = 9V \sin \omega t$, $r_f = 5\Omega$. Find the quiescent point at $V_i = +V_M$ & P_D .

Solⁿ:

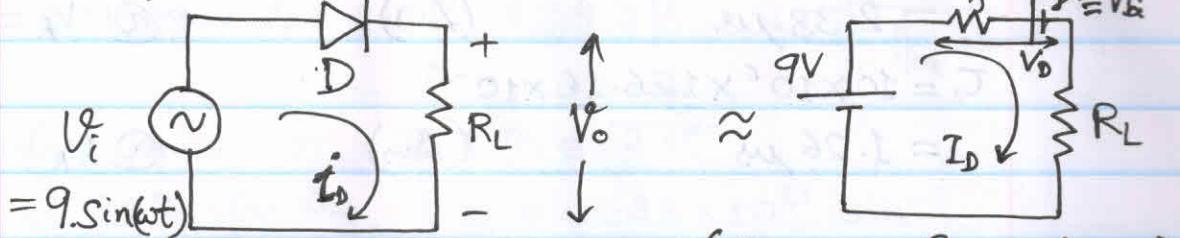

Assume, $f = 50\text{Hz}$

(During forward bias)
=> $V_i = V_M$

By applying KVL in the above ckt., (@ $V_i = +V_M$)

$$I_D = \frac{V_M - V_f}{R_L + r_f} = \frac{9 - 0.3}{3.3 \times 10^3 + 5} = 2.63 \text{ mA}$$

(Ans)

Also,

$$V_D = V_f + I_D \cdot r_f = 0.3 + (2.63 \text{ mA}) \times 5 = 313.15 \text{ mV}$$

(Ans)

$$\begin{aligned} \text{We know, } P_D &= V_D \cdot I_D = (2.63 \text{ mA})(313.15 \text{ mV}) \\ &= 823.58 \mu\text{W} \quad (\text{Ans}) \end{aligned}$$

9. Find the DC load line for the above problem.

Solⁿ: Load line intersects the V-I characteristics:

$$@ V_i = +V_M ; \text{ x-axis: } V_{F_{\max}} = V_M = 9V$$


$$\text{y-axis: } I_y = \frac{V_{F_{\max}}}{R_L + r_f} = \frac{9}{3.3k + 5} = 2.72 \text{ mA}$$

$$@ V_i = -V_M ; \text{ x-axis: } V_{F_{\min}} = -V_M = -9V = V_R = V_D$$

$$\text{y-axis: } I_y = i_D = I_S [e^{\frac{V_D}{r_f}} - 1]$$

$$\text{Assume, } I_S = 10^{-14} \text{ A.}$$
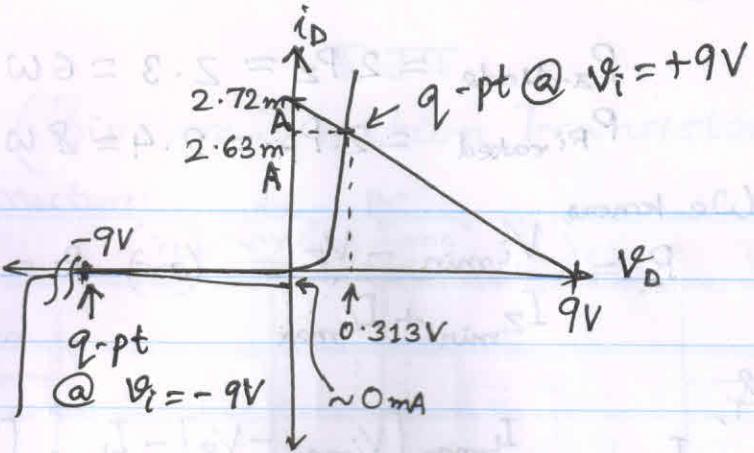
$$\Rightarrow I_y = 10^{-14} \left[e^{\frac{-9}{2 \times 26 \text{ mV}}} - 1 \right] = 0 \text{ mA}$$



10. A full-wave rectifier is operated at a 50Hz AC with an input of $12 \sin \omega t$. If a load resistance is $2.2\text{k}\Omega$ & allowed ripple voltage is 0.5V , calculate the value of a filter capacitor.

Solⁿ: $V_m = 12\text{V}$, $f = 50\text{Hz}$, $V_r = 0.5\text{V}$, $R_L = 2.2\text{k}\Omega$, let $V_f = 0.7\text{V}$

We know,

$$C_{\text{filter}} = \frac{V_m - V_f}{2f \cdot R_L \cdot V_r}$$


$$= \frac{12 - 0.7}{2 \times 50 \times 2.2 \times 10^3 \times 0.5} = 102 \mu\text{F}$$

(Ans)

Now, voltage rating of Filter is: $\geq 2 \cdot V_m$
 $= 25\text{V}$ (Ans)

11. Draw a zener voltage regulator. Assume, $V_i = 10$ to 14V , $I_L = 0$ to 200mA , $V_L = 6\text{V}$. Design the ckt.

Solⁿ:

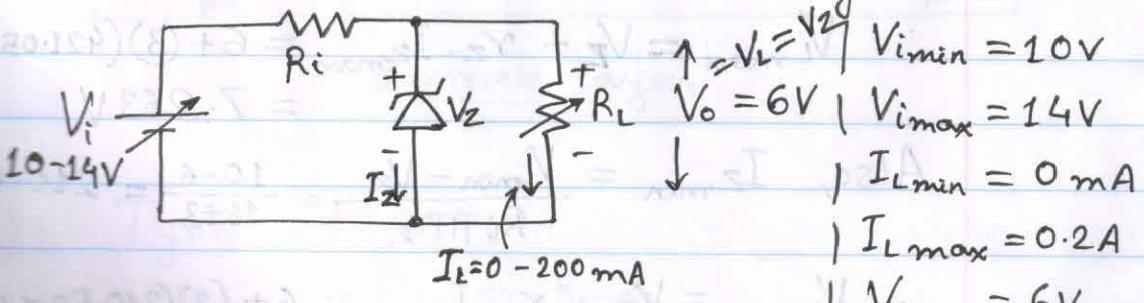

We know, $V_Z = V_L = 6\text{V}$

~~$$I_{D_{\text{max}}} = \frac{(V_{L_{\text{max}}} - V_{Z_{\text{min}}})}{V_{Z_{\text{min}}}} \geq I_{L_{\text{min}}}$$~~

$$\begin{aligned} P_{z\text{-diode}} &= 2 \cdot P_z = 2 \cdot 3 = 6 \text{ W} \\ P_{R\text{rated}} &= 2 \cdot P_{R_i} = 2 \cdot 4 = 8 \text{ W} \end{aligned} \quad \left. \right\} (\text{Ans})$$

We know,

$$R_i = \frac{V_{i\min} - V_z}{I_{z\min} + I_{L\max}} \quad (\text{or}) \quad R_i = \frac{V_{i\max} - V_z}{I_{z\max} + I_{L\min}}$$

&

$$I_{z\max} = \frac{I_{\max} [V_{i\max} - V_z] - I_{L\min} [V_{i\min} - V_z]}{V_{i\min} - 0.9V_z - 0.1V_{i\max}}$$

$$\Rightarrow I_{z\max} = \frac{0.2[14-6] - 0[10-6]}{10 - (0.9)(6) - (0.1)(14)} = 0.5 \text{ A} \quad (\text{Ans})$$

$$\therefore R_i = \frac{14-6}{0.5+0} = 16 \Omega \quad (\text{Ans})$$

Max. Power loss across R_i is:

$$P_{R_i} = \frac{(V_{i\max} - V_z)^2}{R_i} = \frac{(14-6)^2}{16} = 4 \text{ W} \quad (\text{Ans})$$

$$\text{Now, } I_{z\min} = \frac{V_{i\min} - V_z}{R_i} = \frac{10-6}{16} = 0.25 \text{ A} \quad (\text{Ans})$$

$$P_z = V_z \cdot I_{z\max} = 6 \cdot 0.5 = 3 \text{ W} \quad (\text{Ans})$$

12. Calculate line & load regulation, if $r_z = 3 \Omega$

$$\text{Soln. We know, } I_{z\max} = \frac{V_{i\max} - V_z}{R_i + r_z} = \frac{14-6}{16+3} = 421.05 \text{ mA}$$

$$\therefore V_{L\max} = V_z + r_z \cdot I_{z\max} = 6 + (3)(421.05 \times 10^{-3}) = 7.263 \text{ V}$$

$$\text{Also, } I_{z\min} = \frac{V_{i\min} - V_z}{R_i + r_z} = \frac{10-6}{16+3} = 210.52 \text{ mA}$$

$$\therefore V_{L\min} = V_z + r_z \cdot I_{z\min} = 6 + (3)(210.52 \times 10^{-3}) = 6.631 \text{ V}$$

$$V_o = 6.631 \text{ to } 7.263 \text{ V} \\ @ 10V \quad @ 14V \quad V_i$$

$$I_L = 0 \text{ to } 200 \text{ mA}$$

$$7.263V \quad 6.663V @ V_o$$

12. We know, line regulation or Source regulation:
(cont.)

$$\% \text{ line reg.} = \frac{\Delta V_L}{\Delta V_{i,DC}} \times 100$$

$$= \frac{7.263 - 6.631}{14 - 10} = 15.8\% \quad (\text{Ans})$$

Consider, the effect of change in I_L at $V_i = 14V$:

$$\text{For, } I_L = 0 \text{ mA : } I_Z = \frac{14 - 6}{16 + 3} = 421.05 \text{ mA}$$

$$\therefore V_{L,\text{no-load}} = V_Z + r_Z \cdot I_Z = 6 + (3)(421.05) = 7.263V$$

$$\text{For, } I_L = 200 \text{ mA: } I_Z = \frac{V_{i,\text{max}} - [V_Z + I_Z \cdot r_Z]}{R_i} - I_{L,\text{max}}$$

$$= \frac{14 - [6 + (3)(221.06)]}{16} - 0.2$$

$$= 221.06 \text{ mA}$$

$$\therefore V_{L,\text{full-load}} = V_Z + r_Z I_Z = 6 + (3)(221) = 6.663V$$


We know,

$$\% \text{ load reg.} = \frac{V_{L,\text{no-load}} - V_{L,\text{full-load}}}{V_{L,\text{full-load}}} \times 100$$

$$= \frac{7.263 - 6.663}{6.663} \times 100$$

$$= 9.004\% \quad (\text{Ans})$$

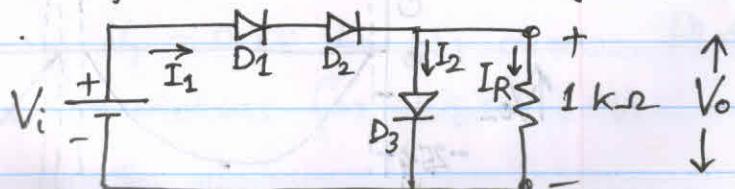13. Consider the ckt. and find the input voltage, if $V_o = 0.6V$
and $I_S = 2 \times 10^{-13} A$.



$$I_2 = I_S \cdot e^{\left(\frac{V_o}{V_T}\right)} = 2 \times 10^{-13} \cdot e^{\left(\frac{0.6}{0.26}\right)} = 2.105 \text{ mA}$$

$$I_R = \frac{V_o}{R} = \frac{0.6}{1k} = 0.6 \text{ mA}$$


$$I_1 = I_2 + I_R = 2.105 \text{ mA} + 0.6 \text{ mA} = 2.705 \text{ mA}$$

$$V_D = V_T \cdot \ln\left(\frac{I_1}{I_S}\right) = 26 \times 10^{-3} \cdot \ln\left(\frac{2.705 \times 10^{-3}}{2 \times 10^{-13}}\right) = 0.6065 \text{ V}$$


$$V_i = 2 \cdot V_D + V_o = 2(0.6065) + 0.6 = 1.81 \text{ V} \quad (\text{Ans})$$

14. Draw the output waveforms of the following ckt:


$$V_S = 26 \cdot \sin(2\pi 60t)$$

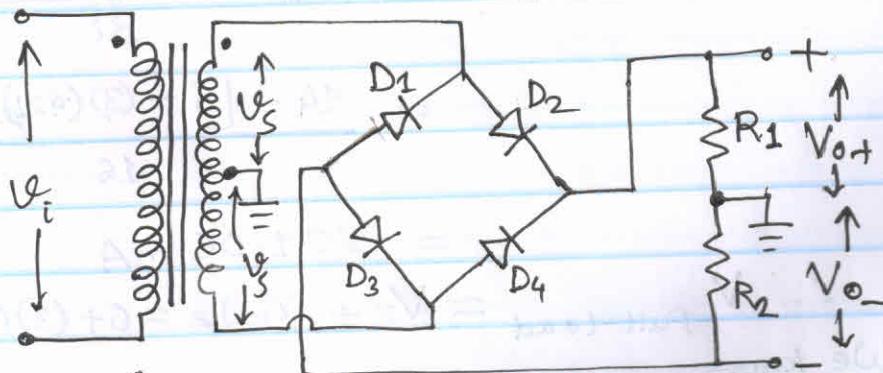


Solⁿ.

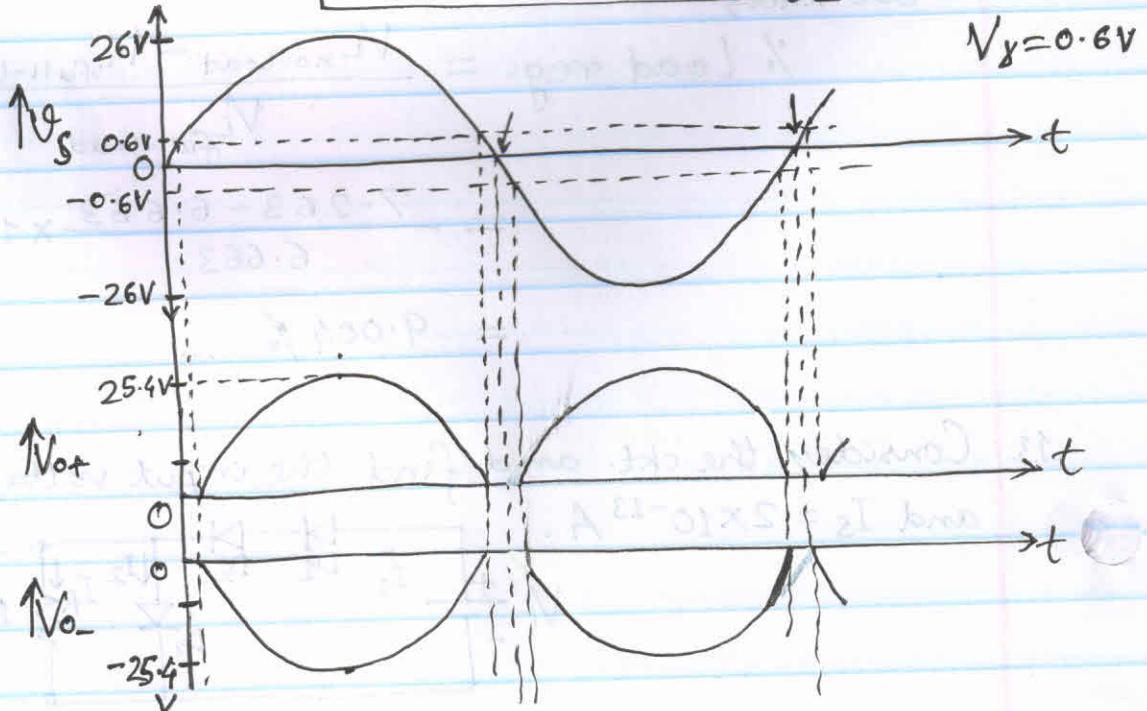

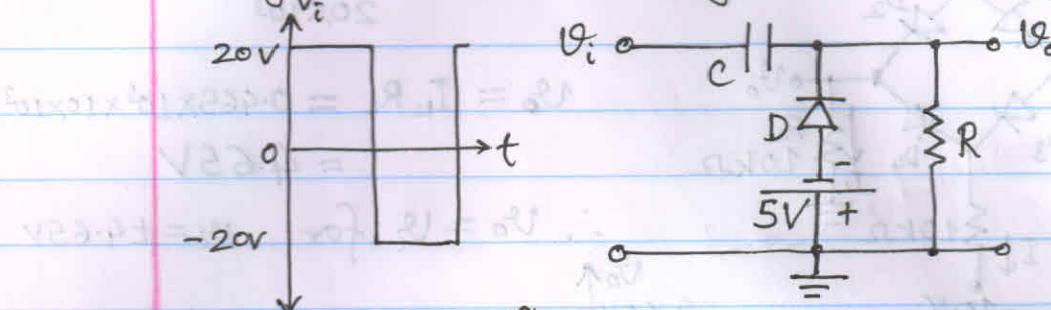- steady-state
15. Draw the output waveform if RC time constant is large and cut-in voltage of the diode is 0V.




Solⁿ.

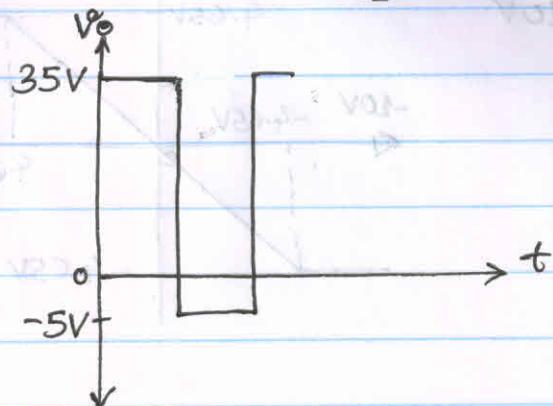

Steps?


16. Draw the ckt. of a bipolar regulated linear power supply by using a center-tapped transformer and a bridge rectifier.

Solⁿ.

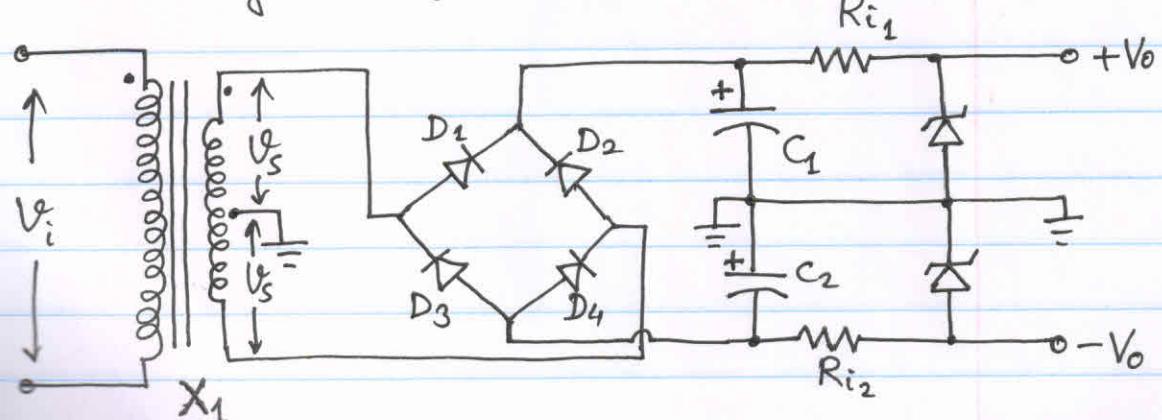

17. For the ckt. shown, $V_F = 0.7V$ for Si diodes. Plot the transfer characteristics for $V_i = \pm 10V$.

Solⁿ:

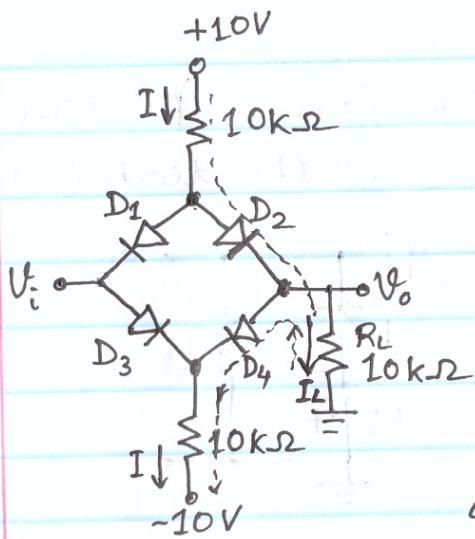


For, $V_i > 0$, D_1 & D_4 are off.

$$I_L = I_i = \frac{10 - 0.7}{20 \times 10^3} = 0.465 \text{ mA}$$

$$V_0 = I_L \cdot R_L = 0.465 \times 10^3 \times 10 \times 10^3 = 4.65 \text{ V}$$

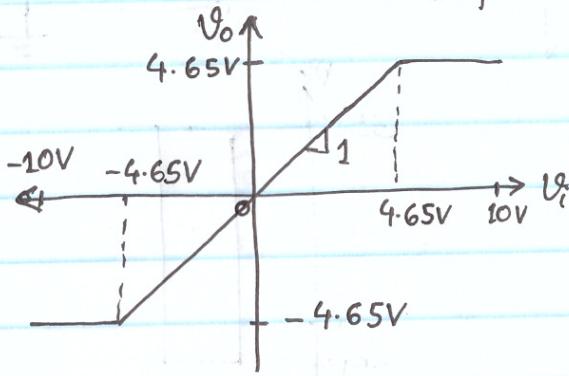$\therefore V_0 = V_i$ for $V_i = \pm 4.65 \text{ V}$




Similarly, while $V_i < 0$, D_2 & D_3 are off.

$$-I_L = I_i = \frac{10 - 0.7}{20 \times 10^3} = 0.465 \text{ mA}$$

$$\&, -V_0 = -I_L \cdot R_L = -4.65 \text{ V}$$

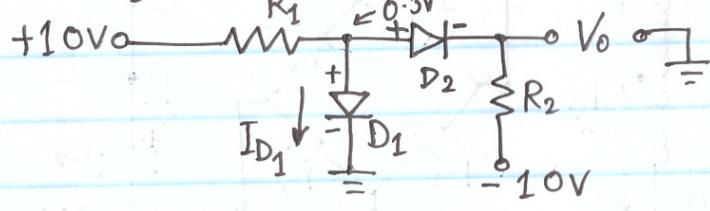
18. Find I_{D_1} & V_0 if $V_g = 0.3 \text{ V}$, $R_1 = 6.8 \text{ k}\Omega$ & $R_2 = 12 \text{ k}\Omega$



Solⁿ: While, D_1 & D_2 are ON, $V_0 = +3 - 0.3 = 0 \text{ V}$ (Ans)

$$\text{Now, } I_{D_1} = \frac{10 - 0.3}{6.8 \times 10^3} = \frac{0 - (-10)}{12 \times 10^3} = 0.593 \text{ mA}$$

(Ans)

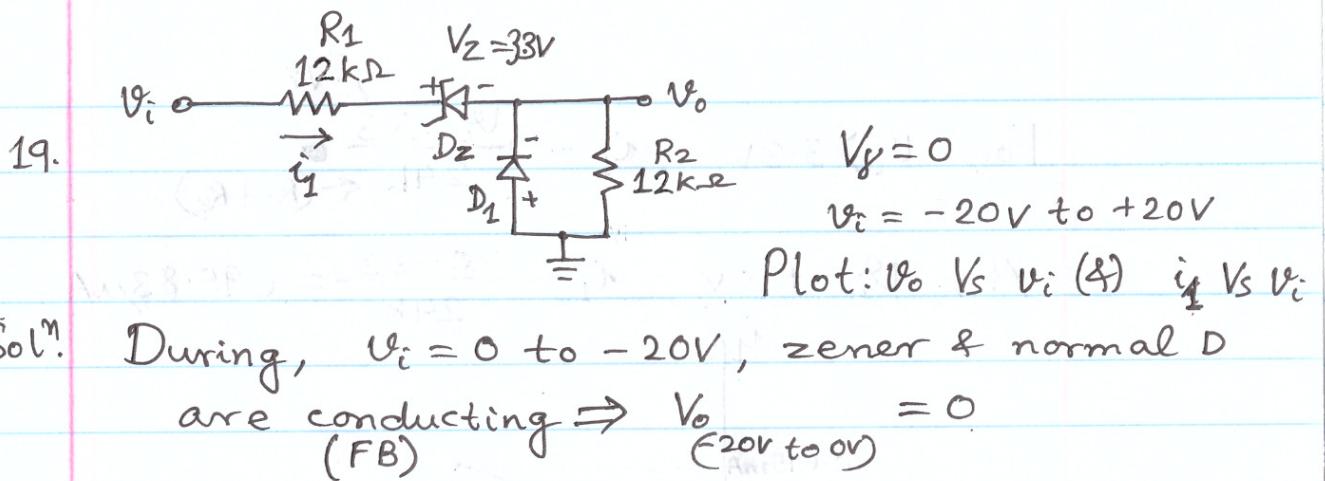

Solⁿ. During, $V_i = 0 \text{ to } -20V$, zener & normal D are conducting $\Rightarrow V_o = 0$

For, $V_i = 0 \text{ to } +3.3V$, zener is in reverse blocking mode (not in breakdown) $\Rightarrow i_1 = 0 \text{ & } V_o = 0$

For, $V_i > 3.3V$, Z-diode enters into brk-dwn state.


$$i_1 = \frac{V_i - 3.3}{12k + 12k} \text{ A}$$

$$\text{&}, \quad V_o = \left[\frac{V_i - 3.3}{12k + 12k} \right] (12k) = \frac{V_i - 3.3}{2}$$

At, $V_i = +20V$,

$$i_1 = \frac{20 - 3.3}{24k} = 695.83 \mu\text{A}$$

$$V_o = 8.35V$$

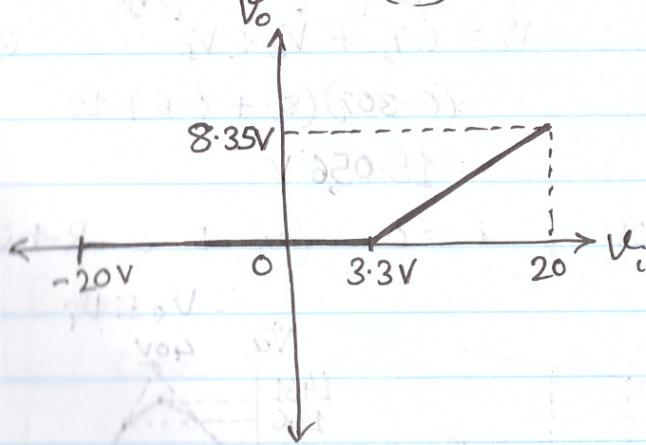


For, $V_i < 0$, $V_o = 0V \text{ & } -i_1 = \frac{0 - V_i}{12k} = \frac{0 - (-20)}{12k}$


$i_1 = -1.666 \text{ mA}$

$$\text{For, } V_i > 3.3V, \quad i_1 = \frac{V_i - 3.3}{24k} \leftarrow (R_1 + R_2) \quad \swarrow V_2$$
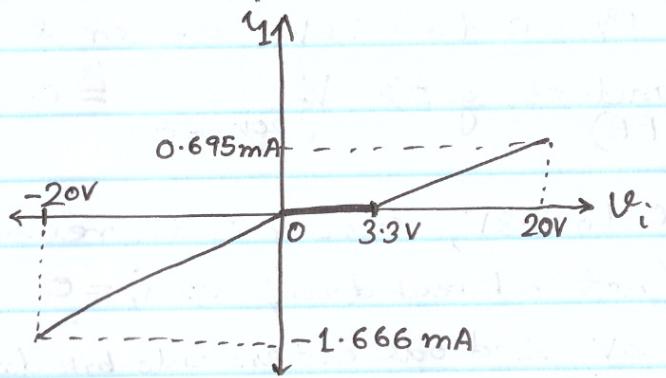
$$\text{At, } V_i = +20V, \quad i_1 = \frac{20 - 3.3}{24k} = 695.83 \mu A$$



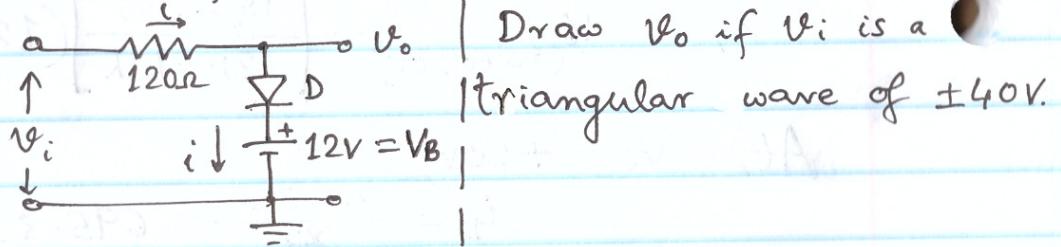20. If $V_y = 0.6V$, $r_f = 8\Omega$, $V_i = \pm 40V$, plot V_o Vs. V_i .



$$\text{Soln. For, } V_i = +40V, \quad i = \frac{40 - 0.6 - 12}{120 + 8} = 214.06 \text{ mA}$$

$$\begin{aligned} V_o &= i \cdot r_f + V_B + V_D \quad @ D_1 \text{ is FB} \\ &= (0.214)(8) + 0.6 + 12 \\ &= 14.31V \end{aligned}$$

For, $V_i = -40V$, $i = 0$ (as D is R-biased)

